

Emec

Experiments :-

- ✓ 1) Measurement of 3- ϕ power using two wattmeter method
- ✓ 2) Perform measurement of reactive power using single wattmeter method.
- ✓ 3) Determination of magnetization characteristics of separately excited DC generator at rated speed.
- 4) To perform Scott connection of transformer.
- ✓ 5) To study parallel operation of transformers.

① 3- ϕ power using two wattmeter method.

Connection :- Current coils of the two wattmeter are connected in series on any 2 lines & corresponding pressure coil is connected ~~to~~ in the ~~these lines and the~~ 3rd line on which no ~~current~~ current coil is connected.

6) To study DC motor starters

7)

① 3- ϕ power by two wattmeter method.

- Connection: Current coil is connected in series with any of the two lines & pressure coil on the 3rd line in which no current coil is connected.
- Current coil:
 - 1) made up of thick wire & fewer no. of turns.
 - 2) Works as ammeter
- Pressure coil:
 - 1) Thin wire & high no. of turns
 - 2) Works as voltmeter
- Wattmeter: Measures active power
$$= VI \cos \phi$$

Derivation :

$$P_{\text{over}} = W_1 + W_2$$

$$\& \quad W = VI \cos \phi \quad (\text{2 wattmeter method} \rightarrow \text{load balanced})$$

~~$$W_1 = \sum L V_L \cos \phi$$~~

$$W_1 = \sum L V_L \cos (30 - \phi)$$

$$W_2 = \sum L V_L \cos (30 + \phi)$$

$$\therefore W_1 + W_2 = \sqrt{3} V_L I_L \cos \phi$$

purely resistive

↓

$$\phi = 0$$

$$\cos \phi = 1$$

Mixed

↓

$$\phi = 60$$

$$\cos \phi = 0.5$$

purely reactive

↓

$$\phi = 90$$

$$\cos \phi = 0$$

• Most versatile method?

↓

2-wattmeter method

• ~~Why not 1 or 3 wattmeter method?~~

Why not 1 or 3 wattmeter method?

- 1 Wattmeter \Rightarrow Simultaneous measurements are not possible because we need to move wattmeter for readings

Ans & In Δ :- As I_L & I_p are different in Δ \therefore we need to connect the wattmeter across phase \therefore we won't have the external connection to measure power.
 ~~Δ connection will be treated to open of circuit (not possible)~~

- Cannot be used in unbalanced condⁿ
- Availability of (N) is must in Δ connection

- 3 Wattmeter \Rightarrow • Not economical
- (Suitable for 3 ϕ 4-wire system) • Same prob. in Δ as 1W method
- Availability of (N) is must in Δ

- Drawbacks of 2 W method :-
- Not suitable for 3 ϕ - 4 wire system

-
- Unit of active power: kW (W in ϕ)
 - Unit of reactive power: KVAR (V in ϕ)
 - Unit of apparent power: KVA (VI)

(2) Reactive power using single wattmeter

Connection: Current coil of wattmeter is connected in any one line & the pressure coils across the other two lines.

• Wattmeter reading = $V_L I_L \cos \phi$

here phase angle b/w V_{LW} & $I_L = 90^\circ - \phi$

$$\therefore W = V_L I_L \cos(90^\circ - \phi)$$

$$W_R = V_L I_L \sin \phi$$

totally 3ϕ reactive power = $\sqrt{3} V_L I_L \sin \phi$
↓
+ve for inductive
-ve for capacitive

(3) Magnetizing characteristics of DC ~~shunt~~ generator.


→ To draw open circuit characteristic curve

- DC generator is an electrical machine that convert mechanical energy of a prime mover into direct electrical energy

(It uses ϕ generated by machine to establish current which gives rise to magnetic field)

Prime mover - machine that convert energy into work.
eg - Turbines

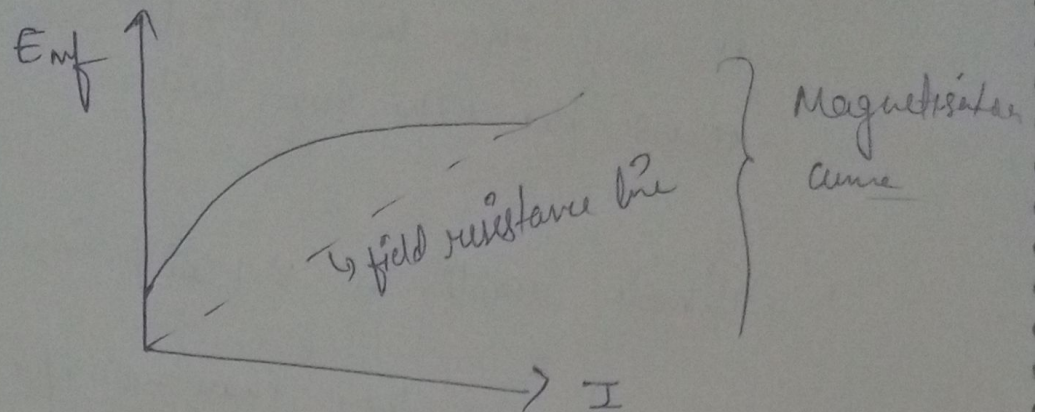OC characteristics :- Relation b/w induced emf at no load and field current.




Why bending of curve?

When there is current flowing in the field winding, the emf induced due to residual flux is present in the machine. If field current \uparrow , flux \uparrow linearly resulting into linear \uparrow in emf but after a certain value of current, the saturation Φ causes slower \uparrow of field current which results in bending.

• Critical field resistance :-

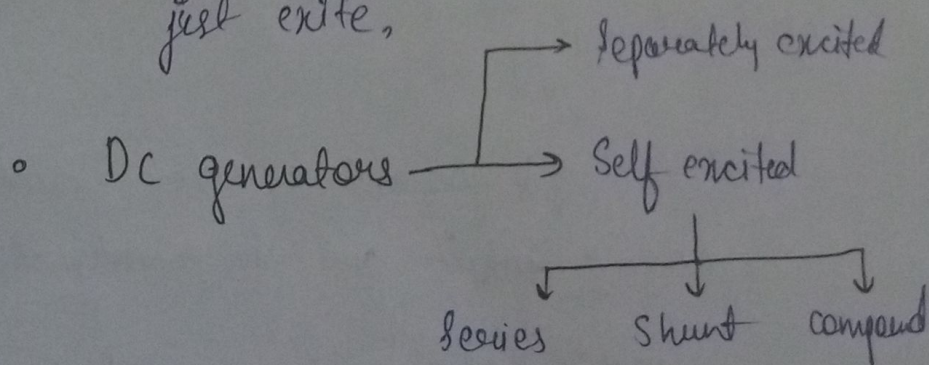The max^o field circuit resistance for a given speed with which the shunt generator could just excite,



④ Parallel operation of two single phase transformers

↳ Power sharing b/w 2 single- ϕ transformers in parallel operation.

Need of Parallel operation :-

When ~~if~~ an existing transformer is not able to withstand the ~~sur~~ sudden increased demand, in that case using that transformer will cause overheating & degrade its expected life. ~~In~~ There, instead of replacing it with ~~an~~ entirely new high capacity unit, it's better to add a smaller unit in parallel to ~~complement~~ the existing one. And now this parallelly connected ~~1~~ unit will be able to ~~be~~ meet the increased demand of power.

Requirements for Parallel connection :-

- Polarity of both transformers must be same
- No load (P) & (S) voltage ~~stands~~ of 2 trans. should ~~not~~ have appreciable diff in magnitude & phase.
- The per unit impedance of 2 trans. on their respective base must be equal.

(5) To perform separation of constant losses in a DC shunt machine.

Constant losses :- Iron losses which include eddy current loss & hysteresis loss.

Eddy current loss :- loss produced by ~~circulating~~ eddy current is known as eddy current loss.

The eddy current induces because of variable magnetic field & conductors.

Hysteresis loss ? The work done by the magnetising force against the internal friction produces & this energy which is wasted in form of heat is called Hysteresis loss.

• Commutator :-

→ It reverses the current dir periodically b/w rotor & external circuit & ∴ generates rotating torque. ↓
DC motor

→ It converts the AC into pulsating DC & insures that current in generator always flows in one direction

↓
DC generator

it's caused by magnetising & demagnetising of the core as current flows in forward & reverse dir.

⑥ Scott connection

↳ Method of ~~connecting~~ connecting two single ϕ transformer to perform 3 ϕ to 2 ϕ conversion.

- One of the transformer is centre tapped & is called main transformer & the other is called teaser transformer.

⇒ ① is tapped $\frac{\sqrt{3}}{2}$ times \Rightarrow Voltages equal

3.3. TYPES OF DC MACHINE

The dc machines are classified into the following group, as per the connection of field winding with armature winding.

1. Separately excited dc machines – The field winding is connected to a separate dc source and has no direct connection with the armature winding.
2. DC shunt machines – The field winding is connected across the terminals of the armature winding. The shunt field coils are wound with many turns of fine wire, as a result the resistance of shunt field winding is appreciably high (of the order of 150 to 250 Ω). The current in the shunt field winding is due to the voltage generated/applied across the armature terminals.
3. DC series machines – The series field winding is connected in series with the armature winding. The series field coils are wound with few turns of wire of large cross-sectional area, as such the resistance of field winding is very low. Series generators will excite only when the load circuit is completed.
4. DC compound machines – Consisting of two field windings i.e. series winding connected in series with the armature winding and shunt winding connected across the armature winding. Both these windings are accommodated on the main pole, as such field magnets are excited partly by shunt field winding and partly by series field winding.